



INSTITUTE OF TECHNOLOGY TRALEE

SUMMER EXAMINATIONS 2011/2012

COMPUTER ARCHITECTURE

Module Code: COMP 61003

CRN: 43828

External Examiner: Mairead O Sullivan

Internal Examiner: Damien Gordon

Duration: 2 Hours

Instructions to Candidates: Answer any *three* questions

Question One

(33 Marks)

(i) Convert the decimal number 62 to its binary **and** hexadecimal equivalent. (8 Marks)

(ii) Show the logic symbol **and** the truth table for: (8 Marks)

(i) AND gate (2 input) (ii) XNOR gate

(iii) Complete the truth table for the expression below: (9 Marks)

$$Z = \overline{A}BC + (C \oplus D)$$

(iv) Draw the circuit for the expression below: (8 Marks)

$$Z = ABD + \overline{C} + D$$

Question Two**(33 Marks)**

- (i) Write an expression for the circuit given below:

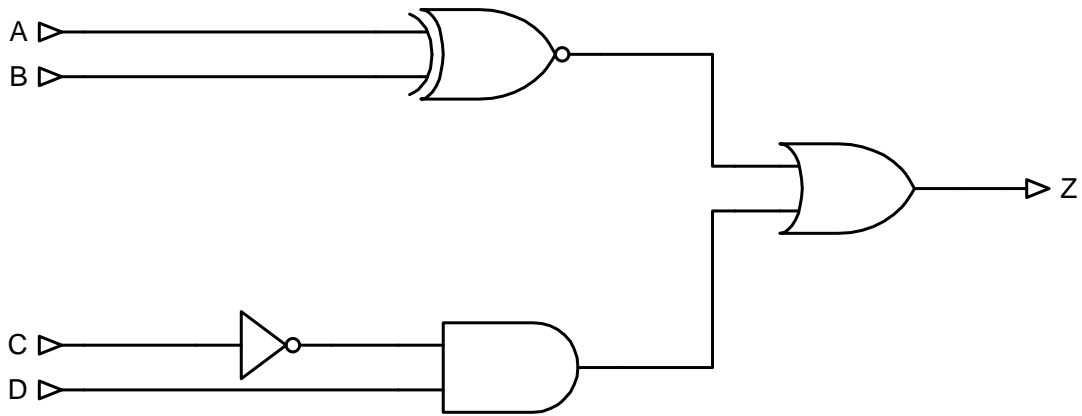


Figure 1

(9 Marks)

- (ii) A majority function of three inputs is TRUE when two or more inputs are TRUE. Use A, B, C as the inputs and let the result be M

- (a) Do the truth table for M
- (b) Write the Equation for M and simplify
- (c) Draw the circuit in its most simplified form.

(12 Marks)

- (iii) Write an expression for Z below. Simplify the expression if possible and draw the circuit.

(12 Marks)

A	B	C	Z
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

Question Three**(33 Marks)**

- (i) Show the truth table for the Full-Adder. Hence or otherwise, write the equation for the Full-Adder and show the logic circuits required to implement it.
(12 Marks)
- (ii) Demonstrate how several Full-Adders can be connected to form a four-bit adder.
(10 Marks)
- (iii) Write a short note on Random Access Memory (RAM), discussing Static-RAM and Dynamic-RAM and highlighting the differences between them. How does ROM differ from RAM?
(11 Marks)

Question Four**(33 Marks)**

- (i) Draw a block diagram of a generic CPU, and write a short paragraph describing the function of each component.
(12 Marks)
- (ii) Write a note on the *Instruction Cycle* of the CPU.
(10 Marks)
- (iii) Show how four flip-flops can be connected to form a serial-in parallel-out register. Show how 1101 would be loaded and read from such a register.
(11 Marks)

Rules of Boolean Algebra

1	$A + 0 = A$
2	$A + 1 = 1$
3	$A \cdot 0 = 0$
4	$A \cdot 1 = A$
5	$A + A = A$
6	$A + \overline{A} = 1$
7	$A \cdot A = A$
8	$A \cdot \overline{A} = 0$
9	$\overline{\overline{A}} = A$
10	$A + AB = A$
11	$A + \overline{A}B = A + B$
12	$(A + B)(A + C) = A + BC$

Laws of Boolean Algebra

Commutative	$A + B = B + A$ $AB = BA$
Associative	$A + (B + C) = (A + B) + C$ $A(BC) = (AB)C$
Distributive	$A(B + C) = AB + AC$

This document was created with Win2PDF available at <http://www.win2pdf.com>.
The unregistered version of Win2PDF is for evaluation or non-commercial use only.